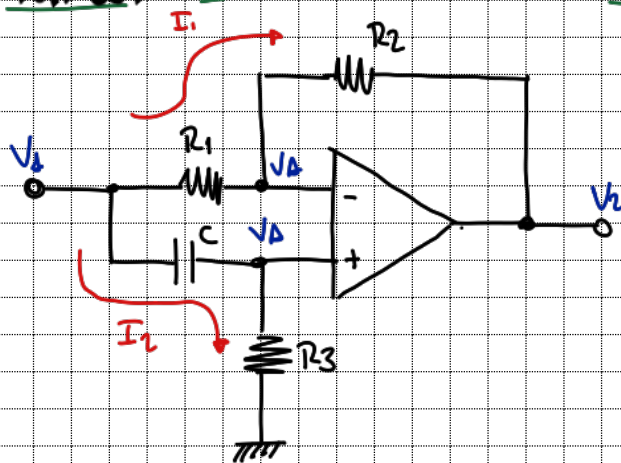


Tarea 0

Montenegro, Maximiliano



$$\frac{V_1 - V_A}{R_1} = I_1 \quad I_1 = \frac{V_A - V_2}{R_2} \quad (2)$$

$$\frac{V_1 - V_A}{\frac{1}{sC}} = I_2 \quad I_2 = \frac{V_A}{R_3} \quad (1)$$

$$(1) \quad (V_1 - V_A)sC = \frac{V_A}{R_3}$$

$$V_1 sC = V_A \left(\frac{1}{R_3} + sC \right)$$

$$V_A = \frac{sC}{\frac{1}{R_3} + sC} V_1$$

$$V_A = \frac{sR_3}{s + \frac{1}{R_3 C}} V_1$$

$$V_A = \frac{s}{s + \frac{1}{R_3 C}} V_1$$

$$(2) \quad \frac{V_1 - V_A}{R_1} = \frac{V_A - V_2}{R_2}$$

$$V_A \left(\frac{1}{R_1} + \frac{1}{R_2} \right) = \frac{V_1}{R_1} + \frac{V_2}{R_2}$$

$$V_A \left(\frac{R_2 + R_1}{R_1 R_2} \right) = \frac{V_1}{R_1} + \frac{V_2}{R_2}$$

$$V_1 \left(\frac{s}{s + \frac{1}{R_3 C}} \right) \left(\frac{R_2 + R_1}{R_1 R_2} \right) = \frac{V_1}{R_1} + \frac{V_2}{R_2}$$

$$V_1 \left(\left(\frac{s}{s + \frac{1}{R_3 C}} \right) \left(\frac{R_2 + R_1}{R_1 R_2} \right) - \frac{1}{R_1} \right) = \frac{V_2}{R_2}$$

$$\frac{V_2}{V_1} = R_2 \left(-\frac{1}{R_1} + \left(\frac{s}{s + \frac{1}{R_3 C}} \right) \left(\frac{R_2 + R_1}{R_1 R_2} \right) \right)$$

$$\frac{V_2}{V_1} = A_v = -\frac{R_2}{R_1} + \left(\frac{s}{s + \frac{1}{R_3 C}} \right) \left(\frac{R_2 + R_1}{R_1} \right)$$

$$A_v = -\frac{R_2}{R_1} + \left(\frac{S}{S + \frac{1}{R_3 C}} \right) \left(\frac{R_2 + R_1}{R_1} \right)$$

$$= -\frac{R_2}{R_1} + \frac{S R_3 C}{S R_3 C + 1} \cdot \frac{R_2}{R_1} + \frac{S R_3 C}{S R_3 C + 1}$$

$$= -\frac{R_2 (S R_3 C + 1)}{R_1 (S R_3 C + 1)} + \frac{R_2 S R_3 C}{R_1 (S R_3 C + 1)} + \frac{S R_3 C}{S R_3 C + 1}$$

$$= \frac{-\cancel{S R_2 R_3 C} - R_2 + R_2 \cancel{S R_3 C} + S R_3 C}{R_1 (S R_3 C + 1)} + \frac{S R_3 C}{S R_3 C + 1} \cdot \frac{R_1}{R_1}$$

$$A_v = \frac{S R_3 C R_1 - R_2}{R_1 (S R_3 C + 1)} = \frac{S R_3 C R_1 - R_2}{S R_3 R_1 C + R_1}$$

$$A_v = \frac{R_3 C R_1}{R_3 C R_1} \cdot \frac{S - \frac{R_2}{R_1 C R_3}}{S + \frac{1}{R_1 C R_3}}$$


$$A_v = \frac{S - \frac{R_2}{R_1 C R_3}}{S + \frac{1}{C R_3}} \quad \frac{1}{C R_3} = p$$

$$s = j\omega$$

$$A_v(s = j\omega) = \frac{j\omega - \frac{R_2}{R_1 C R_3}}{j\omega + \frac{1}{C R_3}}$$


$$|A_v(s = j\omega)| = \frac{\sqrt{\left(\frac{R_2}{R_1 C R_3}\right)^2 + \omega^2}}{\sqrt{\left(\frac{1}{C R_3}\right)^2 + \omega^2}}$$

• Si $\omega = 0 \Rightarrow |A_v| = \frac{\frac{R_2}{R_1 C R_3}}{\frac{1}{C R_3}} = \frac{R_2}{R_1}$

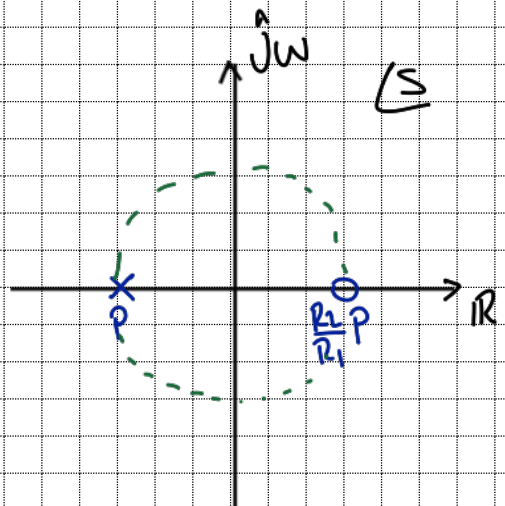

Si $\omega \rightarrow \infty$

$$\lim_{\omega \rightarrow \infty} = \frac{\sqrt{\left(\frac{R_2}{R_1 C R_3}\right)^2 + \omega^2}}{\sqrt{\left(\frac{1}{C R_3}\right)^2 + \omega^2}} \approx \lim_{\omega \rightarrow \infty} \frac{\sqrt{\omega^2}}{\sqrt{\omega^2}} = \lim_{\omega \rightarrow \infty} \frac{|\omega|}{|\omega|} = 1$$

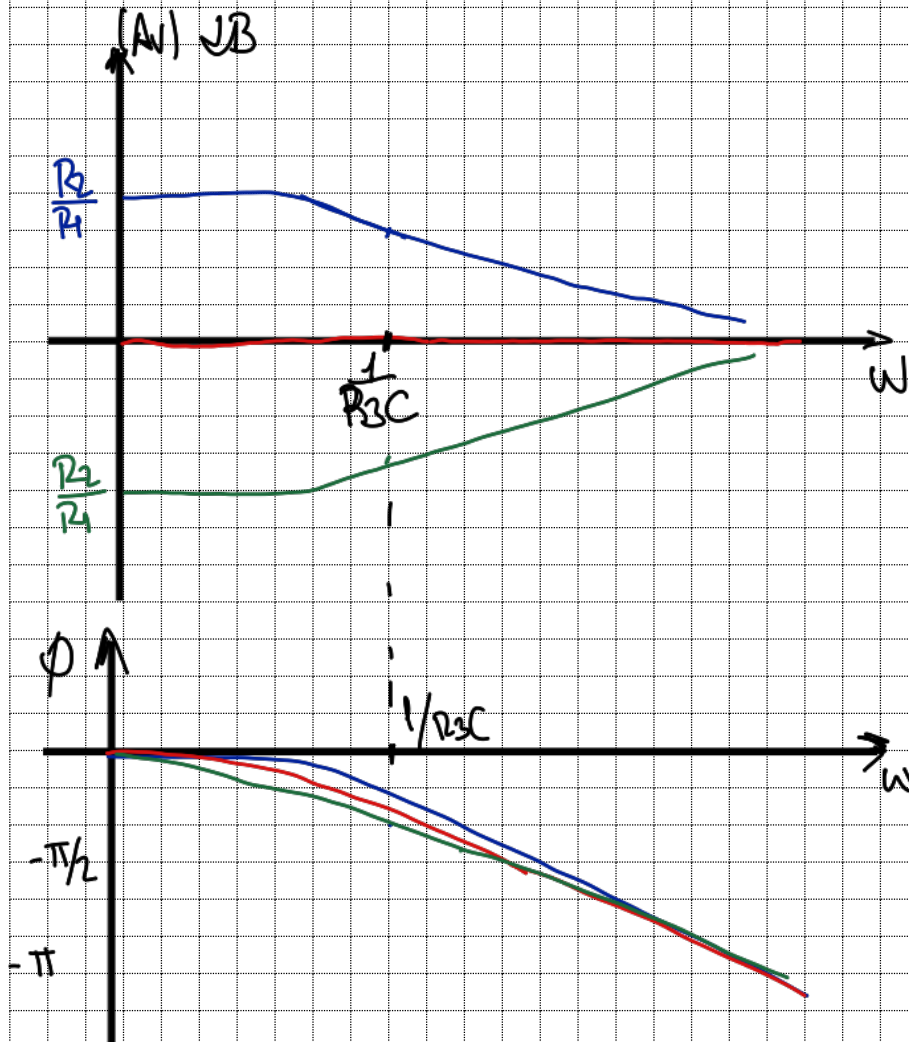

— Si $R_2 > R_1$

— Si $R_2 = R_1$

— Si $R_2 < R_1$

$$\phi: \tan^{-1}\left(-\frac{\omega}{\frac{R_2}{R_1} \frac{1}{C R_3}}\right) - \tan^{-1}\left(\frac{\omega}{\frac{1}{C R_3}}\right)$$

$$\lim_{\omega \rightarrow 0} \phi: 0$$

$$\lim_{\omega \rightarrow \infty} \tan^{-1}\left(\frac{R_2 R_3 C \omega}{R_2}\right) - \tan^{-1}(C R_3 \omega) \rightarrow -\pi/2$$

$$\lim_{\omega \rightarrow \infty} \phi: -\pi$$

$$\begin{aligned} R_2' &= R_2 / R_1 \\ C' &= C / R_1 \end{aligned}$$

$$s = R_3 R_1 C'$$

$$(2) A_v(s) = \left(\frac{s R_3 C R_1 - R_2}{s R_3 R_1 C + R_1} \right) \cdot \frac{1/R_1}{1/R_1}$$

$$A_v(s) = \frac{s R_3 R_1 C' - R_2'}{s R_3 R_1 C' + 1}$$

$$A_v(s) = \frac{s - R_2'}{s + 1}$$

Si $R_2 = R_1$ "Pasa todo"
 $R_2 > R_1$ "Pasa-bajos"
 $R_2 < R_1$ "Pasa-altos"